 



## Figure 9-1 Block Diagram of Static RAM

Table 9-1 Truth Table for Static RAM




$\overline{CS}$	$\overline{OE}$	$\overline{WE}$	Mode	I/O pins
H	X	X	not selected	high-Z
L	H	H	output disabled	high-Z
L	L	H	read	data out
L	X	L	write	data in


## Figure 9-2 Functional Equivalent of a Static RAM Cell

 


**Figure 9-3 Block Diagram of 6116 Static RAM**

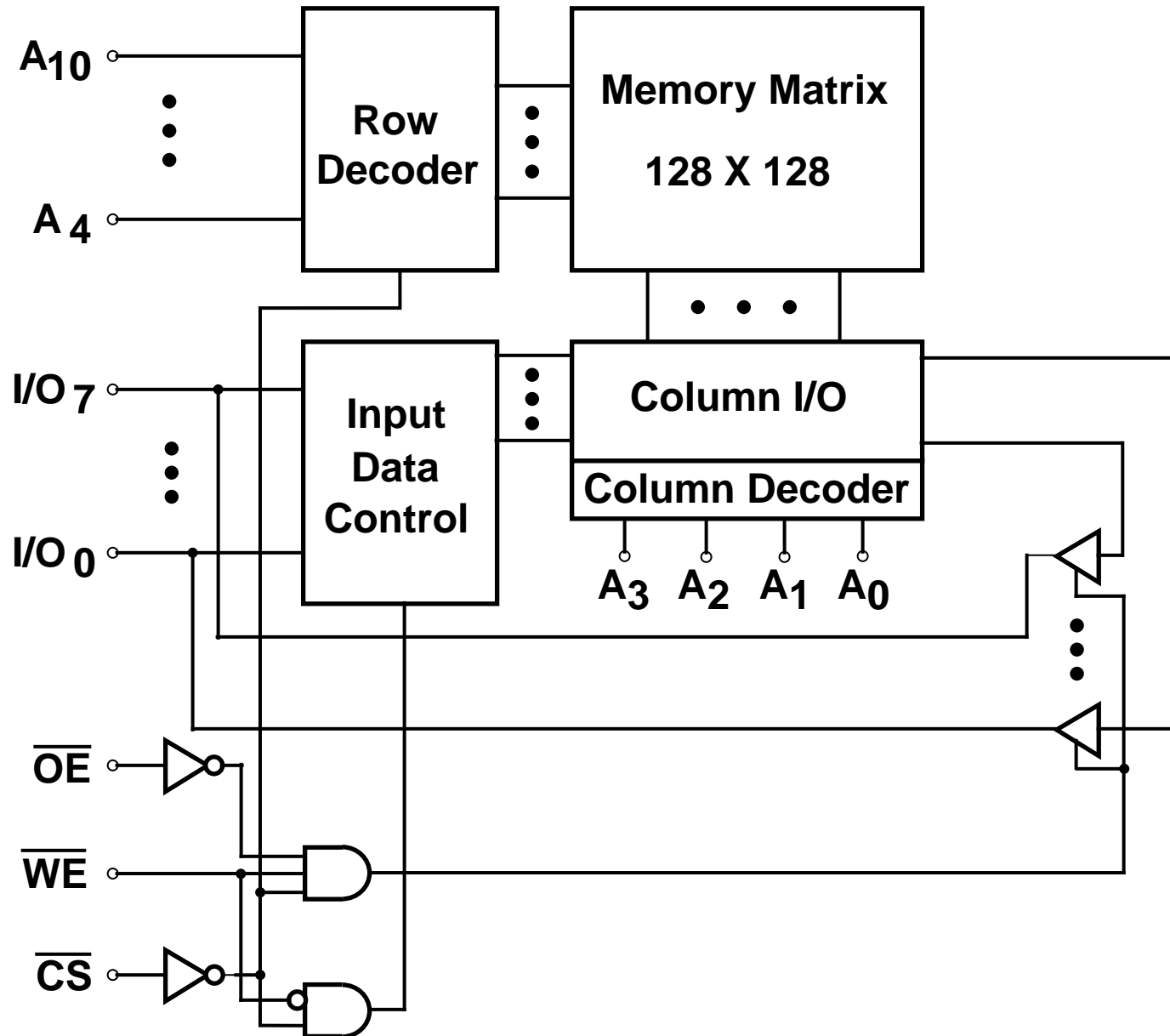

# Figure 9-4 Read Cycle Timing

 

 (a) with  $\overline{CS} = 0$ ,  $\overline{OE} = 0$ ,  $\overline{WE} = 1$




(b) with address stable,  $\overline{OE} = 0$ ,  $\overline{WE} = 1$

**Table 9-2 Timing Specifications for Two Static CMOS RAMs**


Parameter	Symbol	6116-2		43258A-25	
		min	max	min	max
Read Cycle Time	$t_{RC}$	120	–	25	–
Address Access Time	$t_{AA}$	–	120	–	25
Chip Select Access Time	$t_{ACS}$	–	120	–	25
Chip Selection to Output in Low Z	$t_{CLZ}$	10	–	3	–
Output Enable to Output Valid	$t_{OE}$	–	80	–	12
Output Enable to Output in Low Z	$t_{OLZ}$	10	–	0	–
Chip deselection to Output in high Z	$t_{CHZ}$	10*	40	3*	10
Chip Disable to Output in High Z	$t_{OHZ}$	10*	40	3*	10
Output Hold from Address Change	$t_{OH}$	10	–	3	–
Write Cycle Time	$t_{WC}$	120	–	25	–
Chip Selection to End of Write	$t_{CW}$	70	–	15	–
Address Valid to End of Write	$t_{AW}$	105	–	15	–
Address Set Up Time	$t_{AS}$	0	–	0	–
Write Pulse Width	$t_{WP}$	70	–	15	–
Write Recovery Time	$t_{WR}$	0	–	0	–
Write Enable to Output in High Z	$t_{WHZ}$	10*	35	3*	10
Data Valid to End of Write	$t_{DW}$	35	–	12	–
Data Hold from End of Write	$t_{DH}$	0	–	0	–
Output Active from End of Write	$t_{OW}$	10	–	0	–

\*estimated value, not specified by manufacturer

Figure 9-5  $\overline{WE}$ -controlled Write Cycle Timing ( $\overline{OE}=0$ )

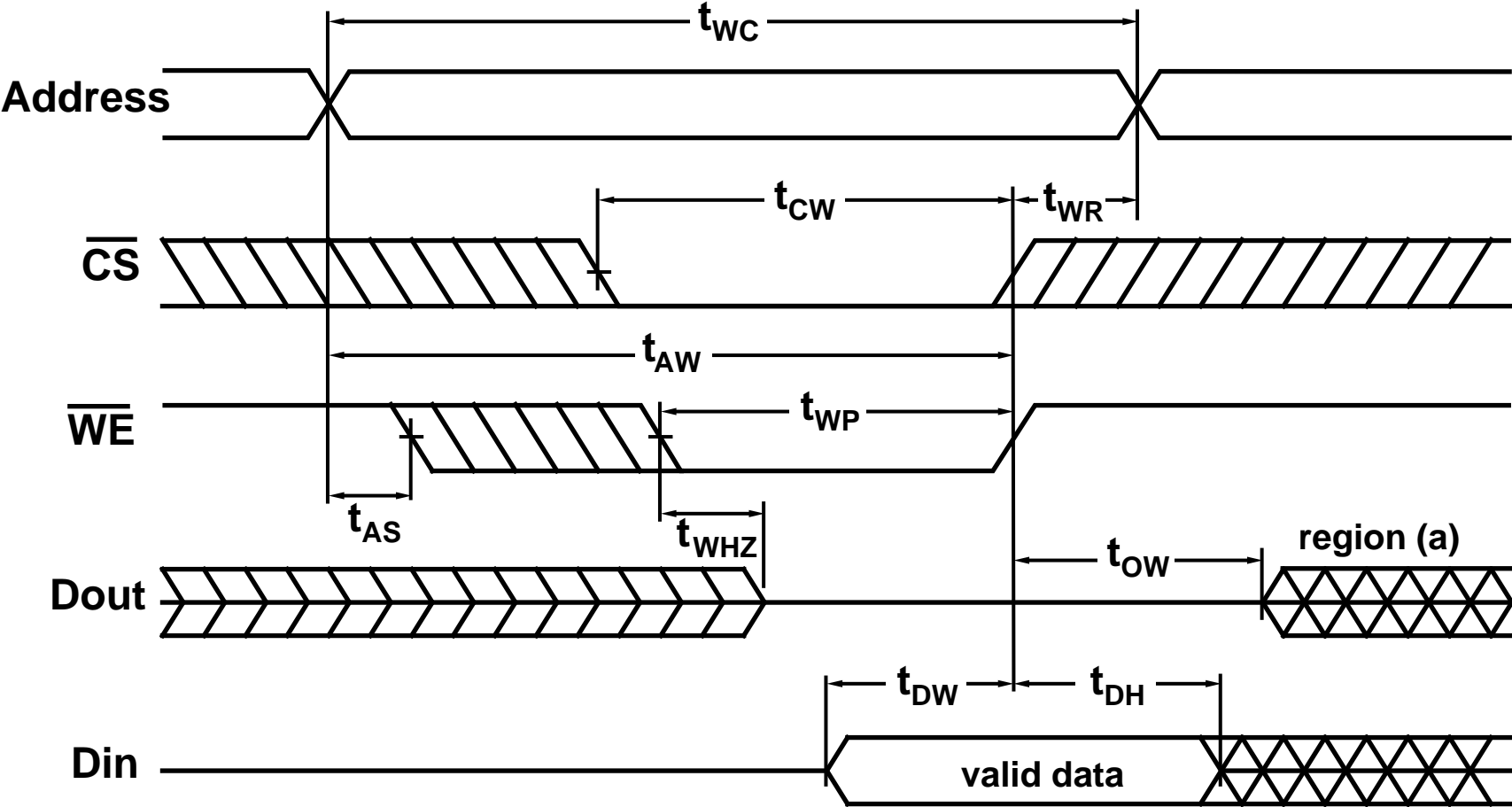


**Figure 9-6  $\overline{\text{CS}}$ -Controlled Write Cycle Timing ( $\overline{\text{OE}}=0$ )**

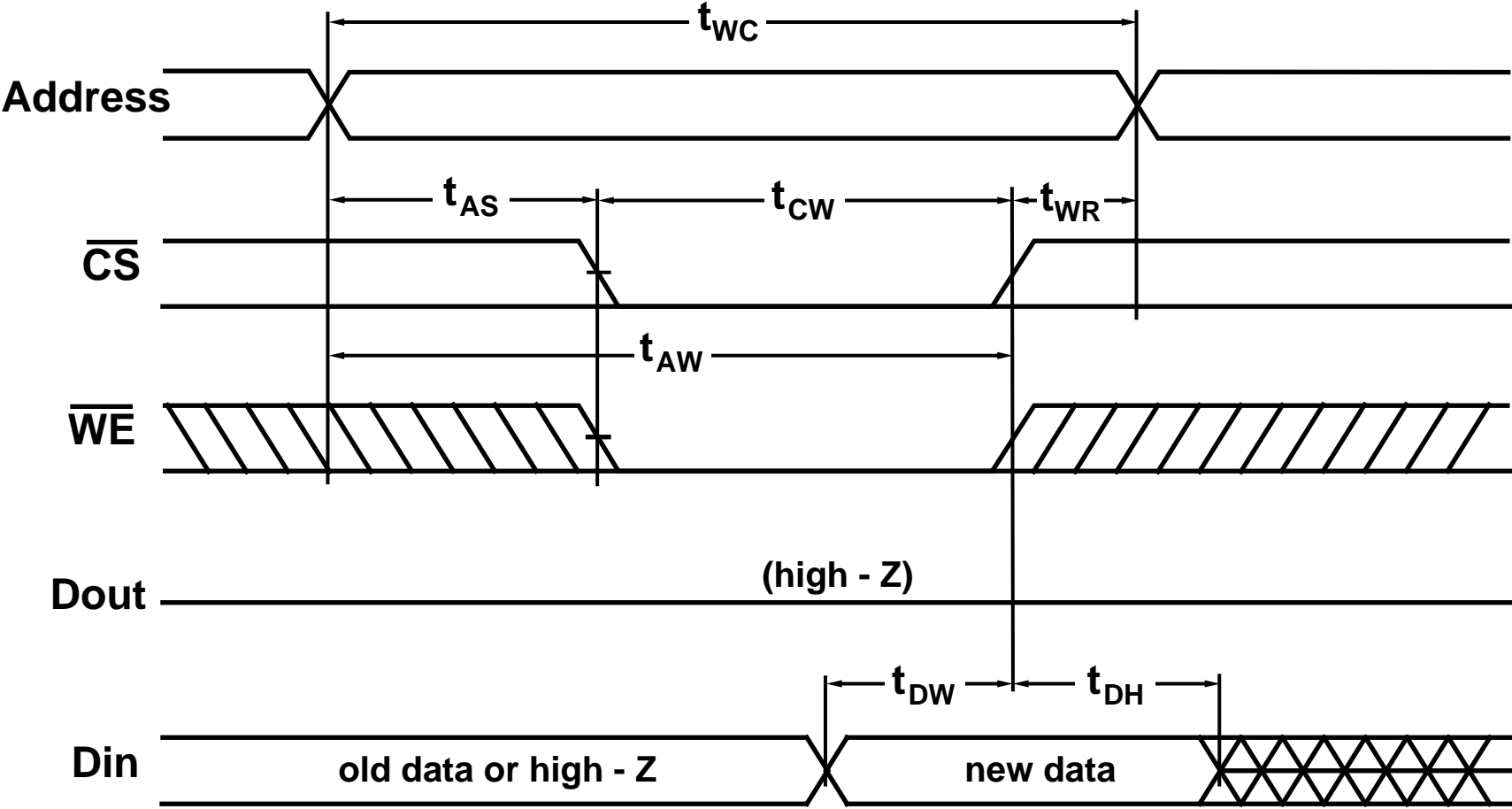


## Figure 9-7 Simple Memory Model

```
library IEEE;
use IEEE.std_logic_1164.all;
library BITLIB;
use BITLIB.bit_pack.all;
entity RAM6116 is
    port(Cs_b, We_b: in bit;
         Address: in bit_vector(7 downto 0);
         IO: inout std_logic_vector(7 downto 0));
end RAM6116;
architecture simple_ram of RAM6116 is
    type RAMtype is array(0 to 255) of std_logic_vector(7 downto 0);
    signal RAM1: RAMtype := (others => (others => '0')); -- Initialize all bits to '0'
begin
    process
    begin
        if Cs_b = '1' then IO <= "ZZZZZZZZ"; -- chip not selected
        else
            if We_b'event and We_b = '1' then -- rising-edge of We_b
                RAM1(vec2int(Address'delayed)) <= IO; -- write
                wait for 0 ns; -- wait for RAM update
            end if;
            if We_b = '1' then
                IO <= RAM1(vec2int(Address)); -- read
            else IO <= "ZZZZZZZZ"; -- drive high-Z
            end if;
        end if;
        wait on We_b, Cs_b, Address;
    end process;
end simple_ram;
```

# Figure 9-8 Block Diagram of RAM System

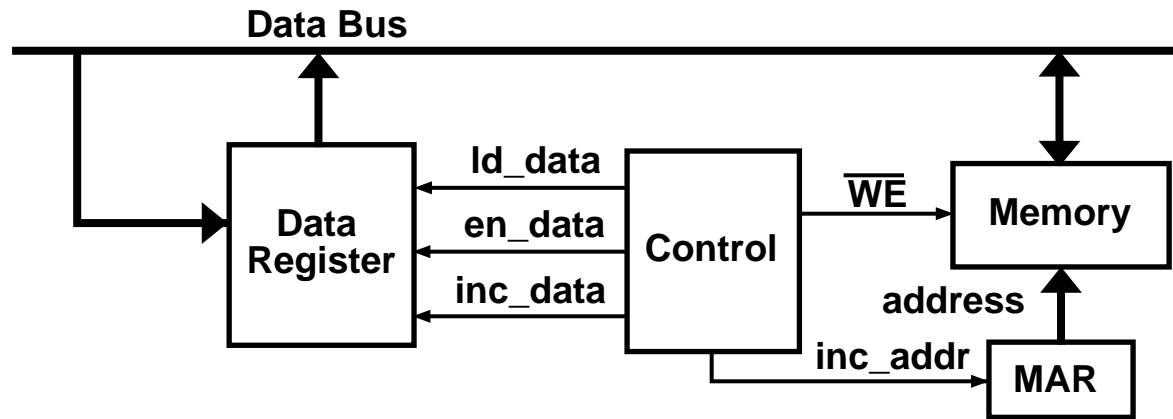

# Figure 9-9 SM Chart of RAM System

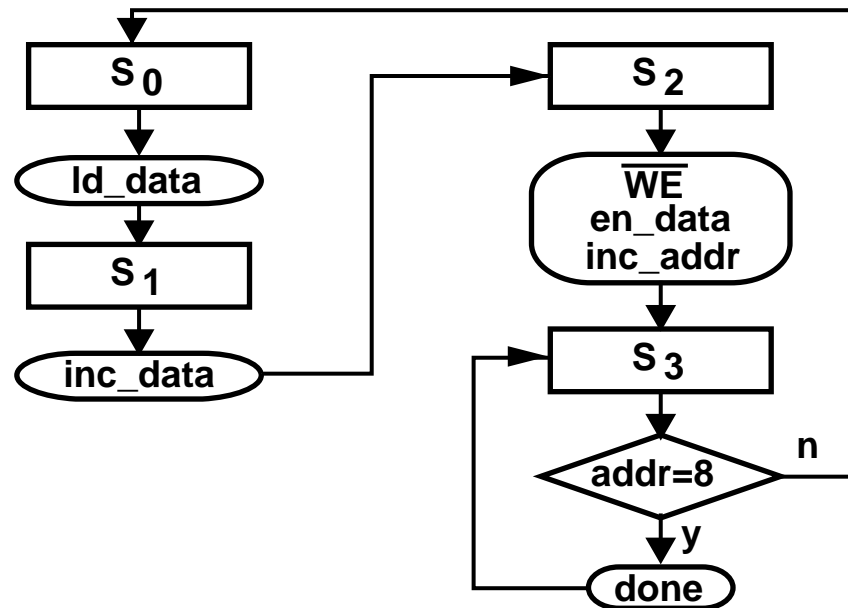



## Figure 9-10(a) Tester for Simple Memory Model

```
library ieee;
use ieee.std_logic_1164.all;
library bitlib;
use bitlib.bit_pack.all;
entity RAM6116_system is
end RAM6116_system;
architecture RAMtest of RAM6116_system is
    component RAM6116 is
        port(Cs_b, We_b: in bit;
            Address: in bit_vector(7 downto 0);
            IO: inout std_logic_vector(7 downto 0));
    end component RAM6116;
    signal state, next_state: integer range 0 to 3;
    signal inc_adrs, inc_data, ld_data, en_data, Cs_b, clk, done: bit;
    signal We_b: bit := '1'; -- initialize to read mode
    signal Data: bit_vector(7 downto 0); -- data register
    signal Address: bit_vector(7 downto 0); -- address register
    signal IO: std_logic_vector(7 downto 0); -- I/O bus

begin
    RAM1: RAM6116 port map(Cs_b, We_b, Address, IO);
    control: process(state, Address)
    begin
        --initialize all control signals (RAM always selected)
        ld_data<='0'; inc_data<='0'; inc_adrs<='0'; en_data <='0';
        done <= '0'; We_b <='1'; Cs_b <= '0';
```

## Figure 9-10(b) Tester for Simple Memory Model

```
--start SM chart here
case (state) is
  when 0 =>   ld_data <= '1'; next_state <= 1;
  when 1 =>   inc_data <= '1'; next_state <= 2;
  when 2 =>   We_b <= '0'; en_data <= '1'; inc_adrs <= '1';
  when 3 =>   if (Address = "00001000") then done <= '1';
               else next_state <= 0;
               end if;

  end case;
end process control;

-- The following process is executed on the rising edge of a clock.
register_update: process
begin
  wait until clk = '1';
  state <= next_state;
  if (inc_data = '1') then data <= int2vec(vec2int(data)+1,8); end if;
  if (ld_data = '1') then data <= To_bitvector(IO); end if;
  if (inc_adrs = '1') then
    Address <= int2vec(vec2int(Address)+1,8) after 1 ns;
    -- delay added to allow completion of memory write
  end if;
end process register_update;

-- Concurrent statements
clk <= not clk after 100 ns;
IO <= To_StdLogicVector(data) when en_data = '1' else "ZZZZZZZZ";
end RAMtest;
```

## Figure 9-11(a) VHDL Timing Model for 6116 Static CMOS RAM

```
-- memory model with timing (OE_b=0)
library ieee;
use ieee.std_logic_1164.all;
library bitlib;
use bitlib.bit_pack.all;

entity static_RAM is
generic (constant tAA: time := 120 ns;      -- 6116 static CMOS RAM
         constant tACS:time := 120 ns;    constant tCLZ:time := 10 ns;
         constant tCHZ:time := 10 ns;    constant tOH:time := 10 ns;
         constant tWC:time := 120 ns;    constant tAW:time := 105 ns;
         constant tWP:time := 70 ns;    constant tWHZ:time := 35 ns;
         constant tDW:time := 35 ns;    constant tDH:time := 0 ns;
         constant tOW:time := 10 ns);

port (CS_b, WE_b, OE_b: in bit;
       Address: in bit_vector(7 downto 0);
       Data: inout std_logic_vector(7 downto 0) := (others => 'Z'));
end Static_RAM;

architecture SRAM of Static_RAM is
type RAMtype is array(0 to 255) of bit_vector(7 downto 0);
signal RAM1: RAMtype := (others => (others => '0'));
```

## Figure 9-11(b) VHDL Timing Model for 6116 Static CMOS RAM

**begin**

RAM: **process**

**begin**

**if** (rising\_edge(WE\_b) **and** CS\_b'delayed = '0')

**or** (rising\_edge(CS\_b) **and** WE\_b'delayed = '0') **then**

RAM1(vec2int(Address'delayed)) <= to\_bitvector(Data'delayed); -- write

Data <= **transport** Data'delayed **after** tOW; -- read back after write

-- Data'delayed is the value of Data just before the rising edge

**end if;**

**if** falling\_edge(WE\_b) **and** CS\_b = '0' **then** -- enter write mode

Data <= **transport** "ZZZZZZZZ" **after** tWHZ;

**end if;**

**if** CS\_b'event **and** OE\_b = '0' **then**

**if** CS\_b = '1' **then** -- RAM is deselected

Data <= **transport** "ZZZZZZZZ" **after** tCHZ;

**elsif** WE\_b = '1' **then** -- read

Data <= "XXXXXXXX" **after** tCLZ;

Data <= **transport** to\_stdlogicvector(RAM1(vec2int(Address)))

**after** tACS;

**end if;**

**end if;**

**if** Address'event **and** CS\_b = '0' **and** OE\_b = '0' **and** WE\_b = '1' **then** --read

Data <= "XXXXXXXX" **after** tOH;

Data <= **transport** to\_stdlogicvector(RAM1(vec2int(Address)))

**after** tAA;

**end if;**

**wait on** CS\_b, WE\_b, Address;

**end process** RAM;

## Figure 9-11(c) VHDL Timing Model for 6116 Static CMOS RAM

```
check: process
begin
    if NOW /= 0 ns then
        if address'event then
            assert (address'delayed'stable(tWC)) -- tRC = tWC assumed
            report "Address cycle time too short" severity WARNING;
        end if;

-- The following code only checks for WE_b controlled write:
        if rising_edge(WE_b) and CS_b'delayed = '0' then
            assert (address'delayed'stable(tAW))
            report "Address not valid long enough to end of write"
            severity WARNING;
            assert (WE_b'delayed'stable(tWP))
            report "Write pulse too short"
            severity WARNING;
            assert (Data'delayed'stable(tDW))
            report "Data setup time too short"
            severity WARNING;
            wait for tDH;
            assert (Data'last_event >= tDH)
            report "Data hold time too short"
            severity WARNING;
        end if;
    end if;
    wait on WE_b, address, CS_b;
end process check;
end SRAM;
```

## Figure 9-12(a) VHDL Code for Testing the RAM Timing Model

```
library IEEE;
use IEEE.std_logic_1164.all;
library BITLIB;
use BITLIB.bit_pack.all;

entity RAM_timing_tester is
end RAM_timing_tester;

architecture test1 of RAM_timing_tester is

    component static_RAM is
    port (CS_b, WE_b, OE_b: in bit;
        Address: in bit_vector(7 downto 0);
        Data: inout std_logic_vector(7 downto 0));
    end component Static_RAM;

    signal Cs_b, We_b: bit := '1'; -- active low signals
    signal Data: std_logic_vector(7 downto 0) := "ZZZZZZZZ";
    signal Address: bit_vector(7 downto 0);
```

## Figure 9-12(b) VHDL Code for Testing the RAM Timing Model


```
begin
  SRAM1: Static_RAM port map(Cs_b, We_b, '0', Address, Data);
  process
  begin
    wait for 100 ns;
    Address <= "00001000";           -- write(2) with CS pulse
    Cs_b <= '0'; We_b <= transport '0' after 20 ns;
    Data <= transport "11100011" after 140 ns;
    Cs_b <= transport '1' after 200 ns;
    We_b <= transport '1' after 180 ns;
    Data <= transport "ZZZZZZZZ" after 220 ns;
    wait for 200 ns;

    Address <= "00011000";           -- RAM deselected
    wait for 200 ns;


    Address <= "00001000";           -- Read cycles
    Cs_b <= '0';
    wait for 200 ns;
    Address <= "00010000";
    Cs_b <= '1' after 200 ns;
    wait for 200 ns;

    Address <= "00011000";           -- RAM deselected
    wait for 200 ns;
  end process;
end test1;
```
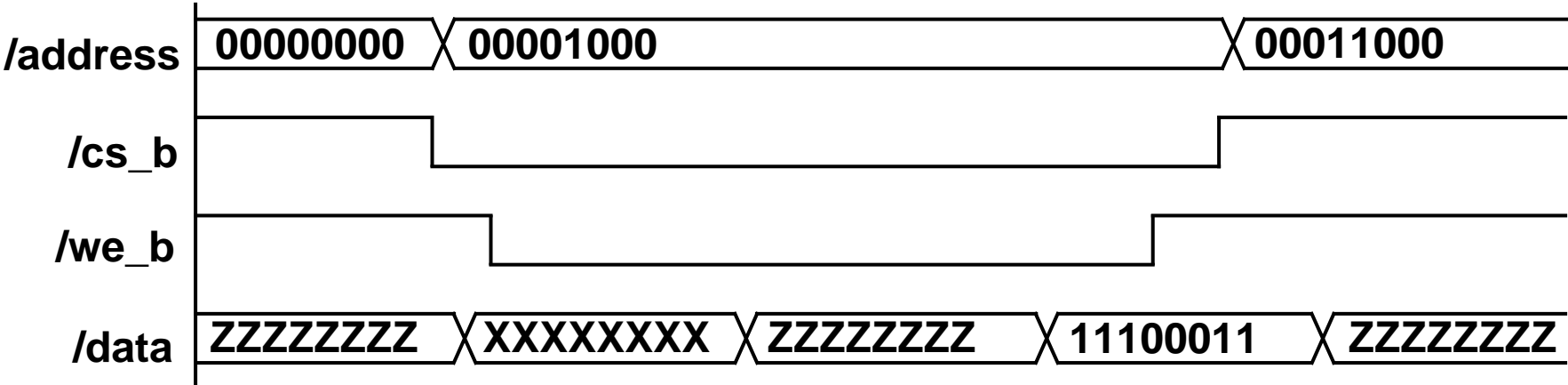
# Figure 9-13 Test Results for RAM Timing Model




(a) Write cycle

 


(b) Two read cycles




**Figure 9-14 Microprocessor Bus Interface**

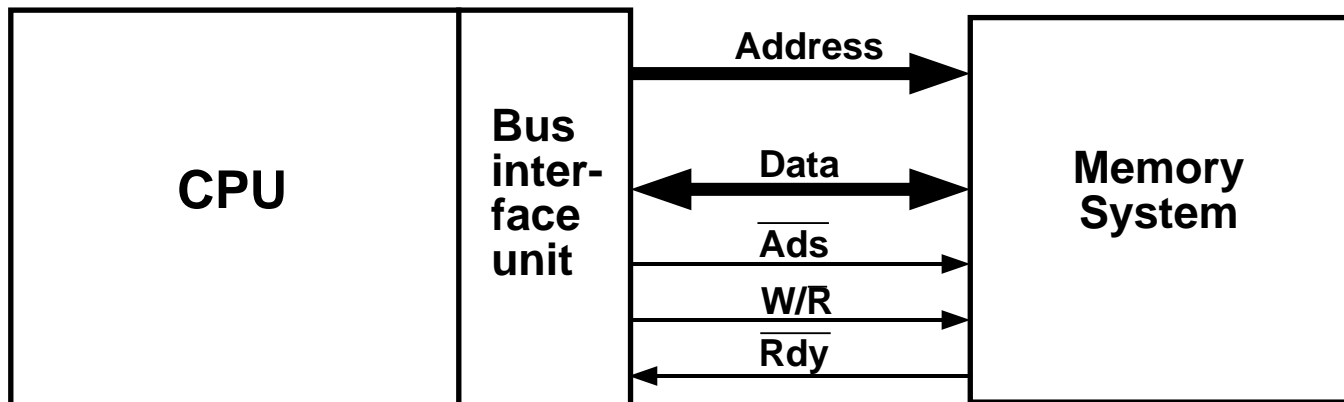


# Figure 9-15 Intel 486 Basic 2-2 Bus Cycle

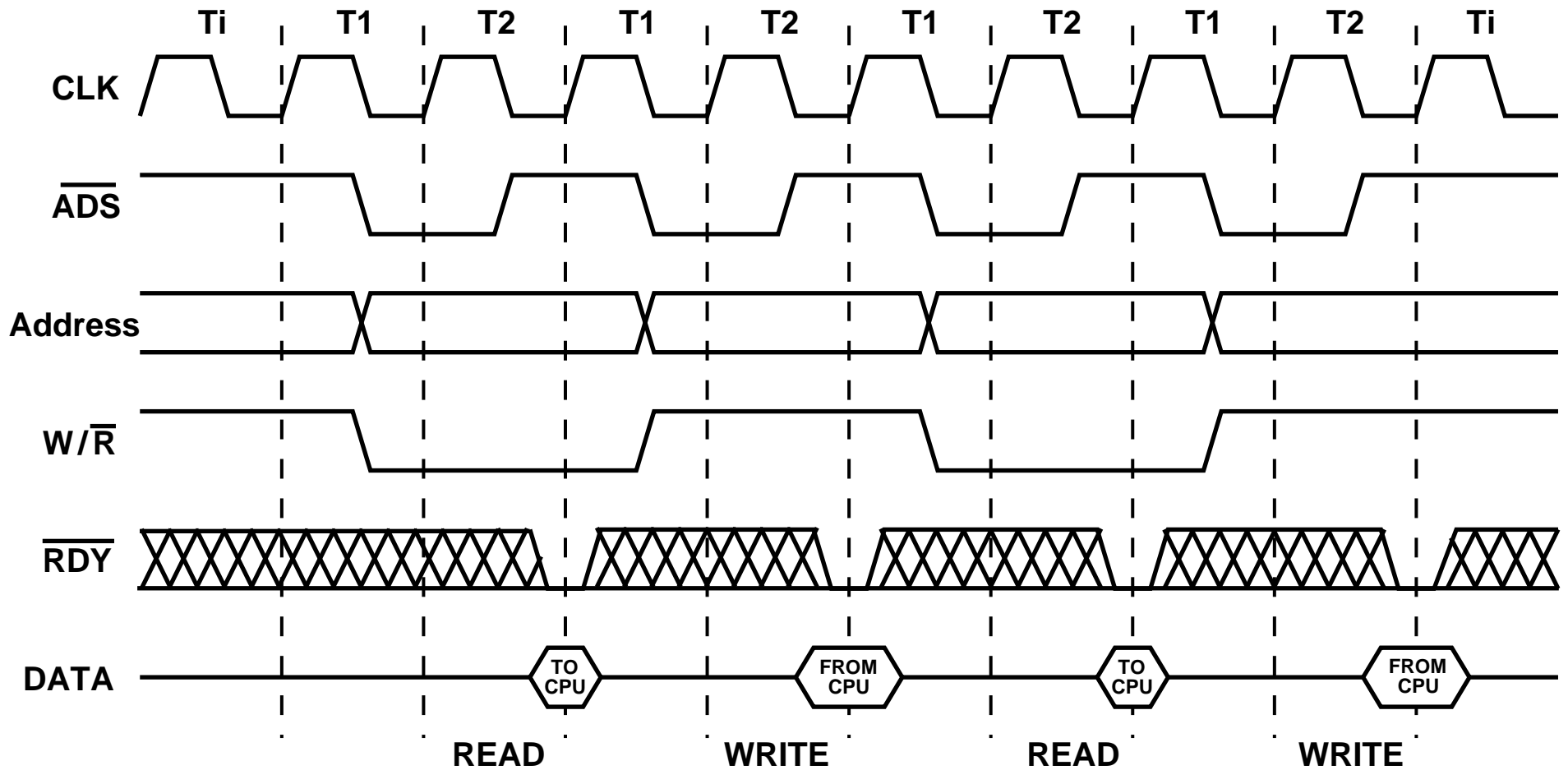


**Figure 9-16 Intel 486 Basic 3-3 Bus Cycle**

 


**Figure 9-17 Simplified 486 Bus Interface Unit**

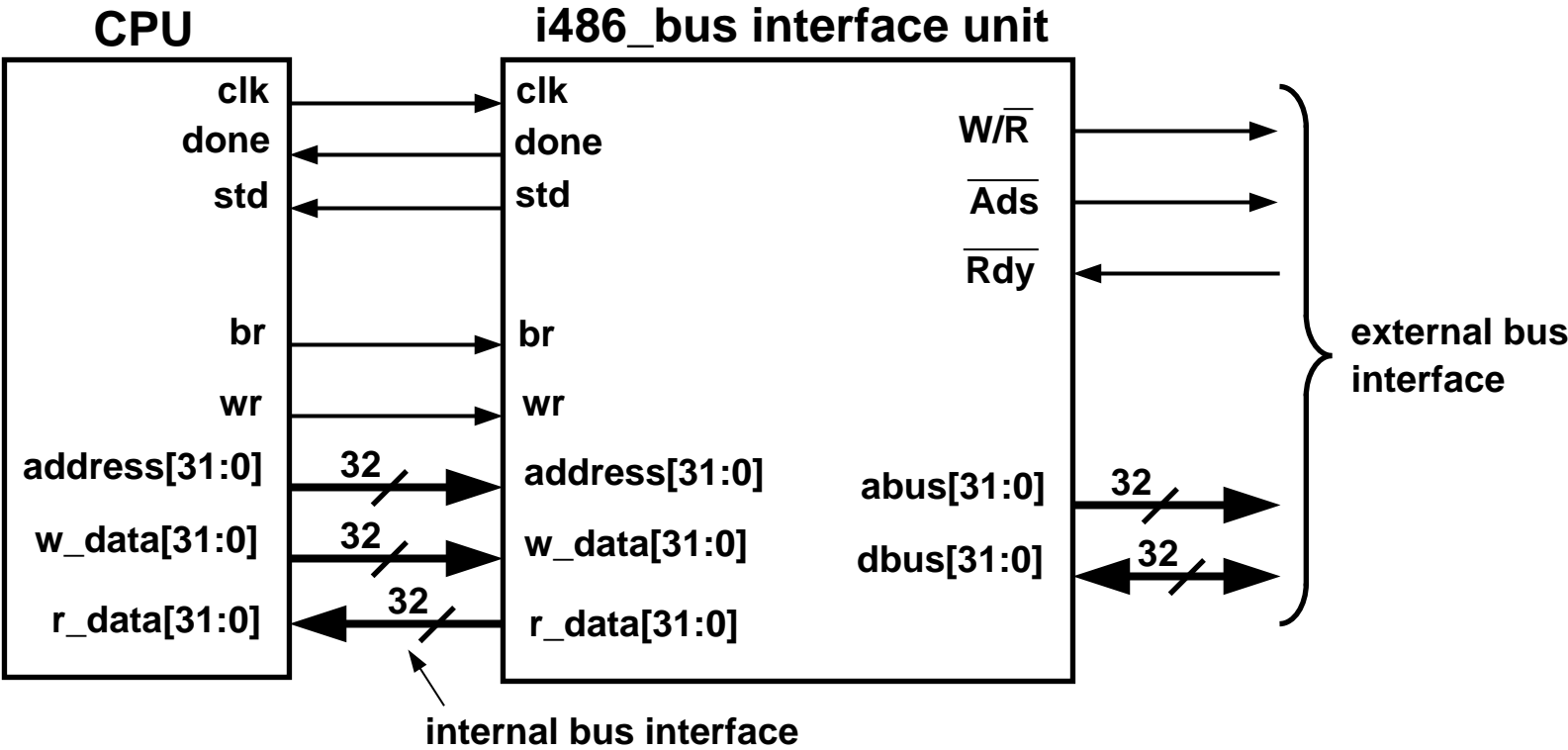

# Figure 9-18 SM Chart for Simplified 486 Bus Interface

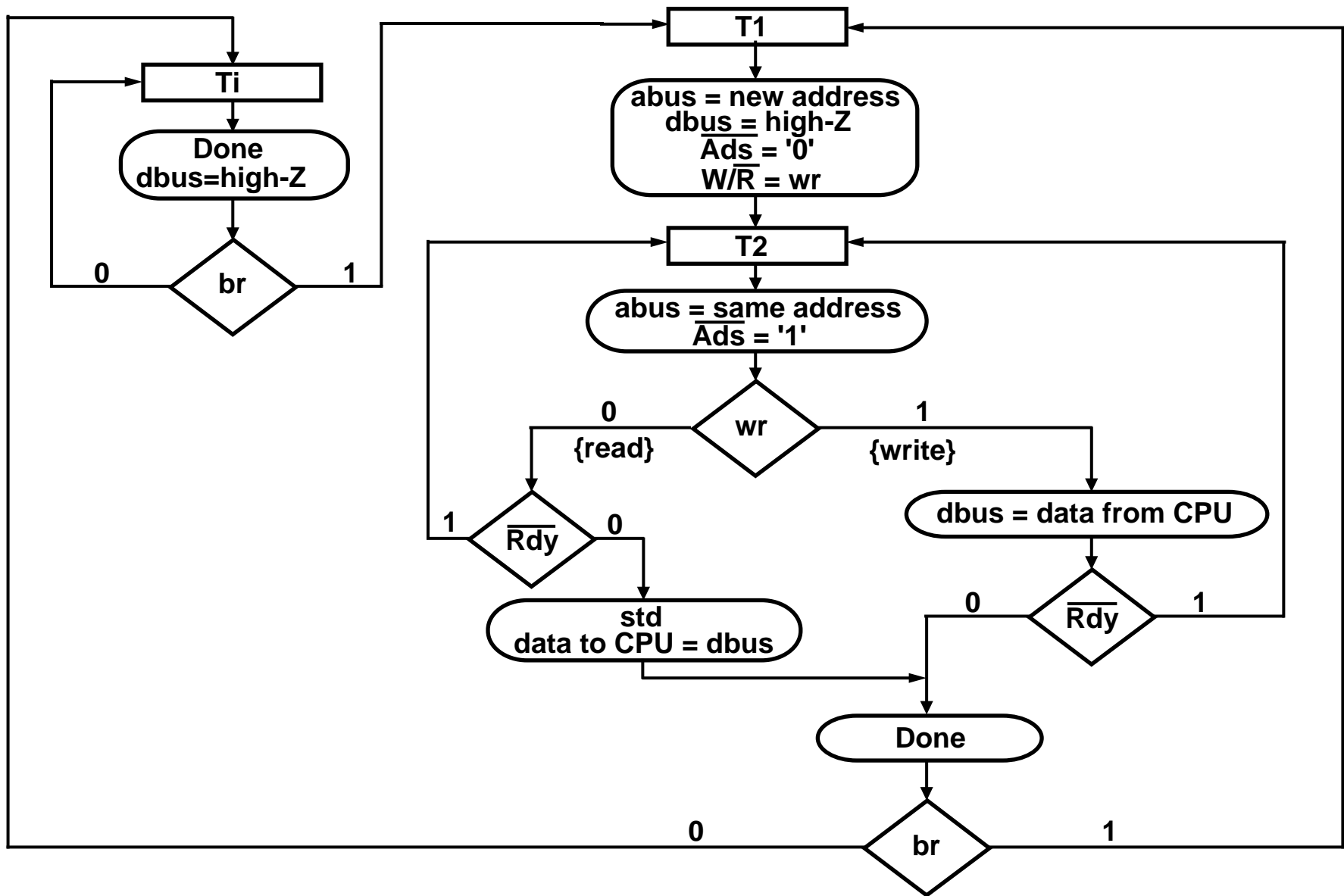


**Figure 9-19 486 Setup and Hold Time Specifications**

 

**Figure 9-20**

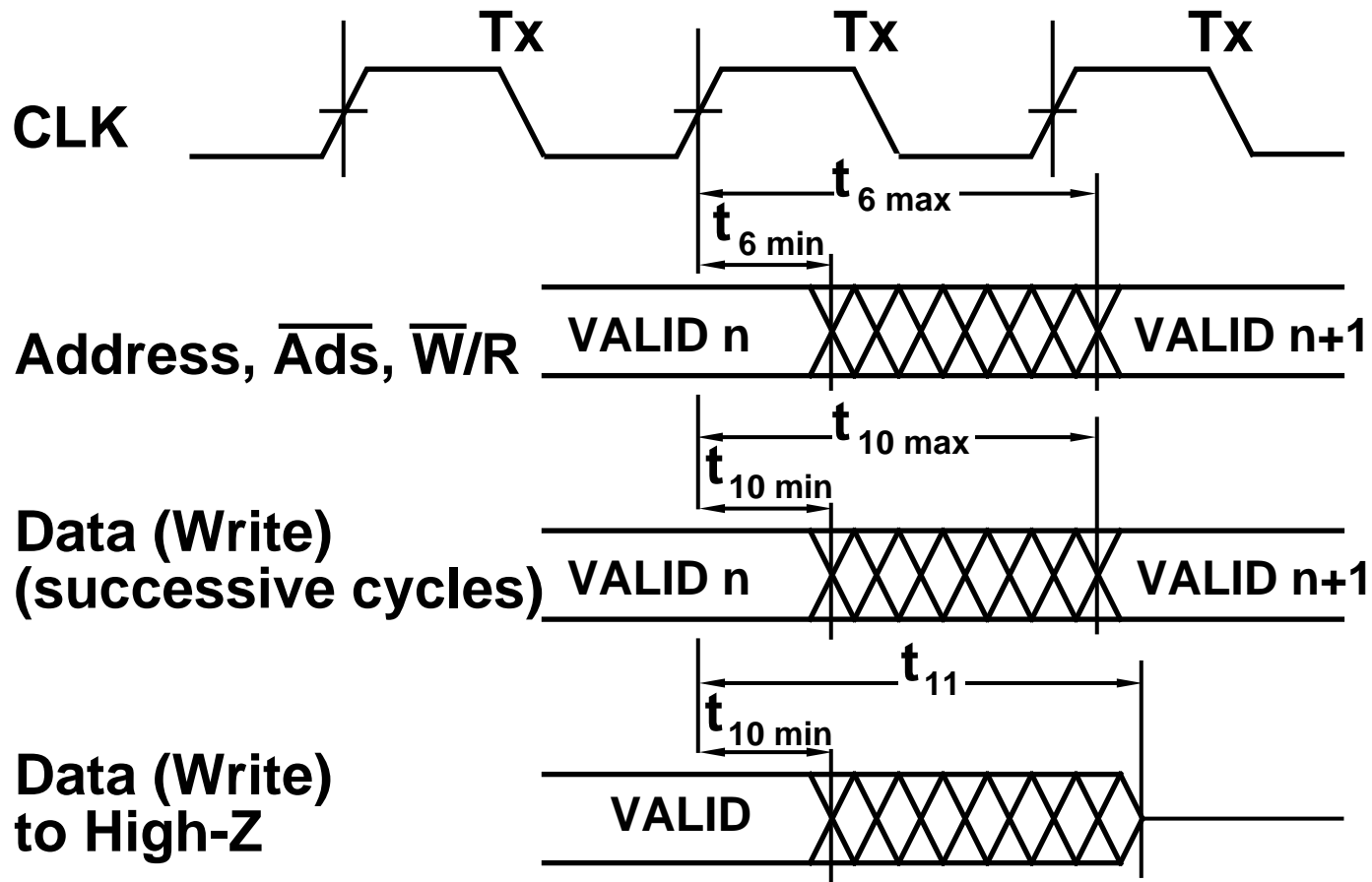**486 Bus Timing Specifications for Address and Data Changes**



## Figure 9-21(a) VHDL Model for 486 Bus Interface Unit

```
LIBRARY ieee;
use ieee.std_logic_1164.all;
entity i486_bus is
    generic (-- These specs are for the i486DX 50
        constant t6_max:time:=12 ns;    constant t10_min:time:=3 ns;
        constant t10_max:time:=12 ns;  constant t11_max:time:=18 ns;
        constant t16_min:time:=5 ns;   constant t17_min:time:=3 ns;
        constant t22_min:time:=5 ns;   constant t23_min:time:=3 ns);
    port (--external interface
        abus: out bit_vector(31 downto 0);
        dbus: inout std_logic_vector(31 downto 0) := (others => 'Z');
        w_rb, ads_b: out bit := '1';   rdy_b, clk: in bit;
    --internal interface
        address, w_data: in bit_vector(31 downto 0);
        r_data: out bit_vector(31 downto 0); wr, br: in bit; std, done:out bit);
end i486_bus;
_*****

architecture simple_486_bus of i486_bus is
type state_t is (Ti, T1, T2);
signal state, next_state:state_t:=Ti;
_*****

begin
-- The following process outputs the control signals and address of the processor during a
-- read/write operation. The process also drives or tristates the databus depending on the
-- operation type. During the execution of a read/write operation, the done signal is low.
-- When the bus is ready to accept a new request, done is high.
comb_logic: process
```



## Figure 9-21(b) VHDL Model for 486 Bus Interface Unit

**begin**

std <= '0';

**case** (state) **is**

**when** Ti=> done<='1';

**if** (br = '1') **then** next\_state <= T1;

**else** next\_state <= Ti;

**end if;**

dbus <= **transport** (others =>'Z') **after** t10\_min;

**when** T1=> done <= '0';

ads\_b <= **transport** '0' **after** t6\_max; w\_rb <= **transport** wr **after** t6\_max;

abus <= **transport** address **after** t6\_max;

dbus <= **transport** (others =>'Z') **after** t10\_min; next\_state <= T2;

**when** T2=>

ads\_b <= **transport** '1' **after** t6\_max;

**if** (wr = '0') **then** -- read

**if** (rdy\_b = '0') **then**

r\_data <= to\_bitvector(dbus); std <= '1'; done <= '1';

**if** (br = '0') **then** next\_state <= Ti;

**else** next\_state <= T1;

**end if;**

**else** next\_state <= T2;

**end if;**

**else** -- write

dbus <= **transport** to\_stdlogicvector(w\_data) **after** t10\_max;

**if** (rdy\_b = '0') **then**

done<='1';

**if** (br = '0') **then** next\_state <= Ti;

## Figure 9-21(c) VHDL Model for 486 Bus Interface Unit

```
                else next_state <= T1;
                end if;
            else next_state <= T2;
            end if;
        end if;
    end case;
    wait on state, rdy_b, br, dbus;
end process comb_logic;
--*****
--The following process updates the current state on every rising clock edge
seq_logic: process(clk)
begin
    if (clk = '1') then state <= next_state; end if;
end process seq_logic;
--*****
--The following process checks that all setup and hold times are met for all incoming control
-- signals. Setup and hold times are checked for the data bus during a read only.
wave_check: process (clk, dbus, rdy_b)
    variable clk_last_rise:time:= 0 ns;
begin
    if (now /= 0 ns) then
        if clk'event and clk = '1' then -- check setup times
            --The following assert assumes that the setup for RDY
            -- is equal to or greater than that for data
            assert (rdy_b /= '0') OR (wr /= '0') OR
                (dbus'last_event >= t22_min)
            report "i486 bus:Data setup too short"
```

## Figure 9-21(d) VHDL Model for 486 Bus Interface Unit

```
        severity WARNING;
    assert (rdy_b'last_event >= t16_min)
        report "i486 bus:RDY setup too short"
        severity WARNING;
    clk_last_rise := NOW;
end if;
if (dbus'event) then                                -- check hold times
    -- The following assert assumes that the hold for RDY
    -- is equal to or greater than that for data
    assert (rdy_b /= '0') OR (wr /= '0') OR
        (now - clk_last_rise >= t23_min)
        report "i486 bus:Data hold too short"
        severity WARNING;
end if;
if (rdy_b'event) then
    assert (now - clk_last_rise >= t17_min)
    report "i486 bus: RDY signal hold too short"
    severity WARNING;
end if;
end if;
end process wave_check;
end simple_486_bus;
```

# Figure 9-22 486 Bus Interface to Static Ram System



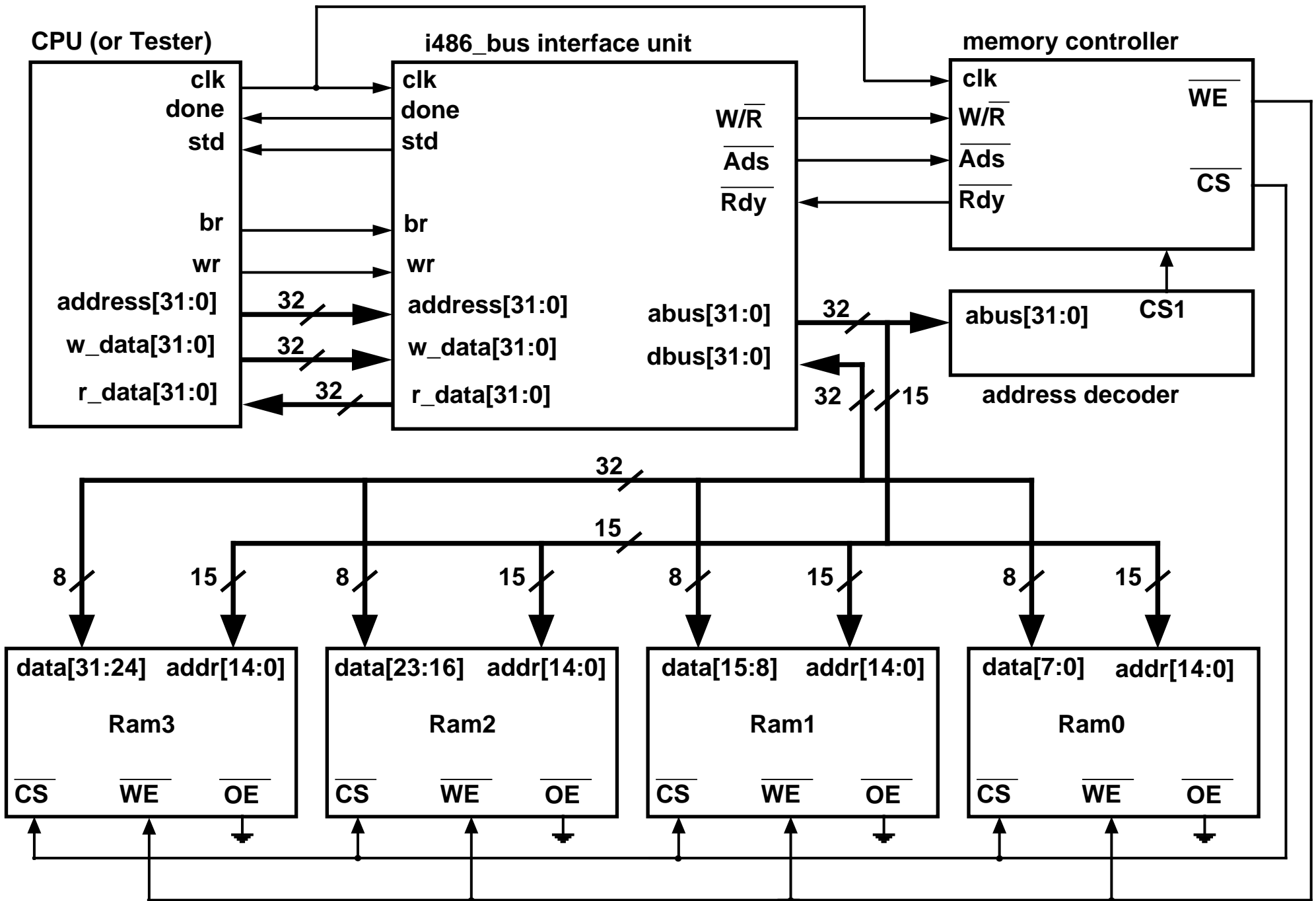



Figure 9-23 Signal Paths for Memory Read

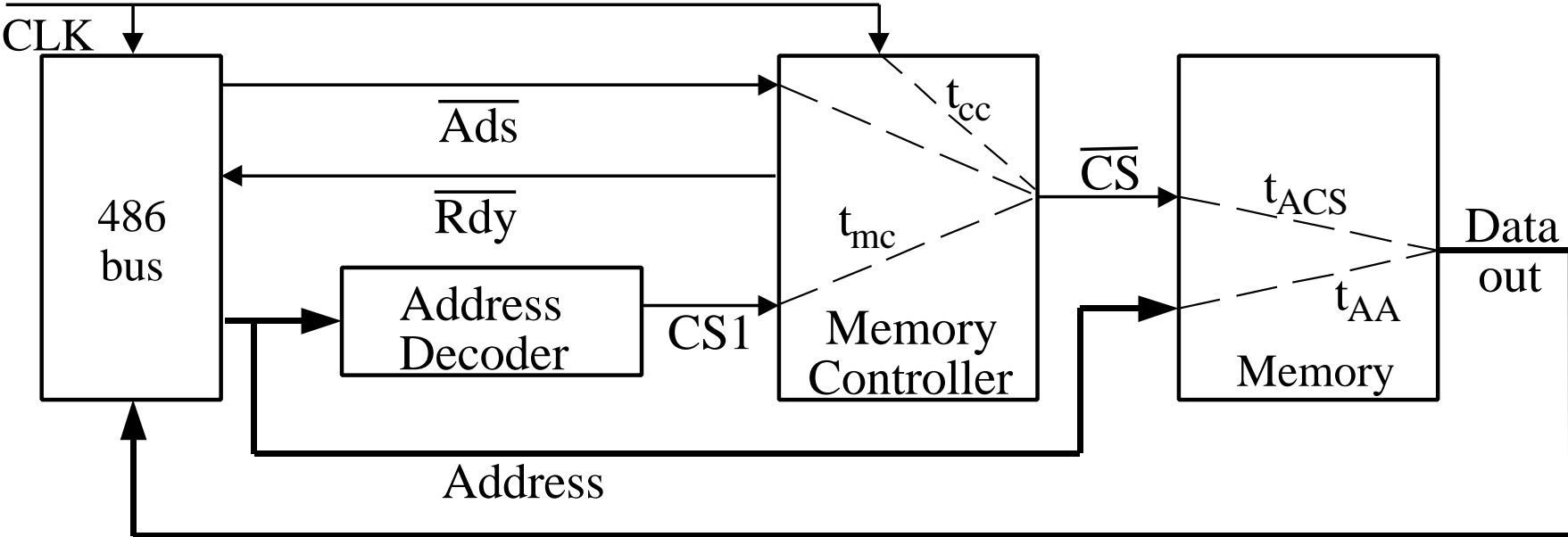


**Figure 9-24 Memory Controller SM Chart for Read Cycles**

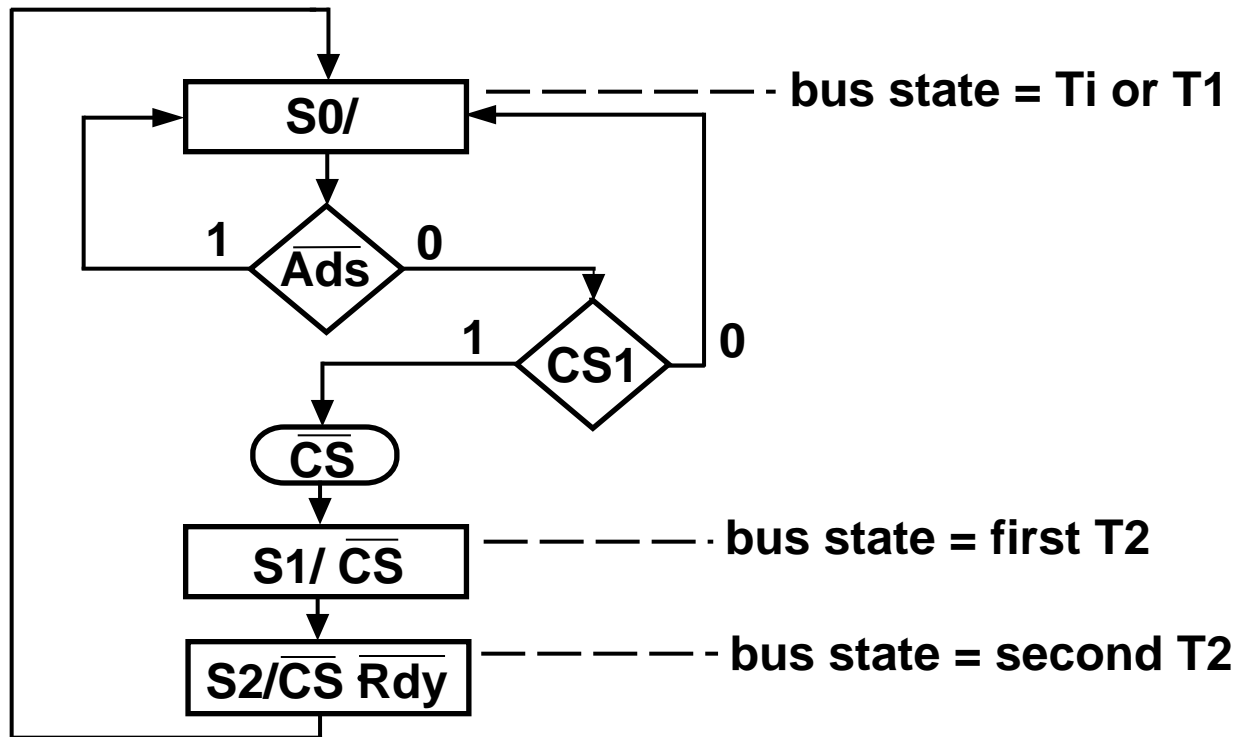

# Figure 9-25 Chip Select Timing for Write to RAM

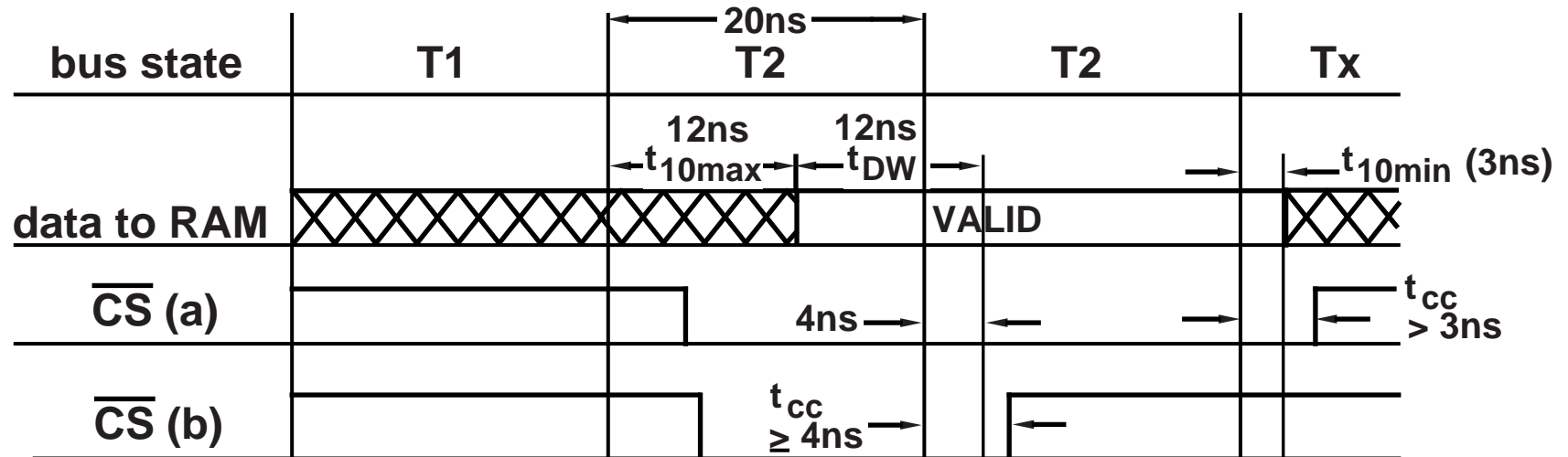

**Figure 9-26 SM Chart of Memory Controller**

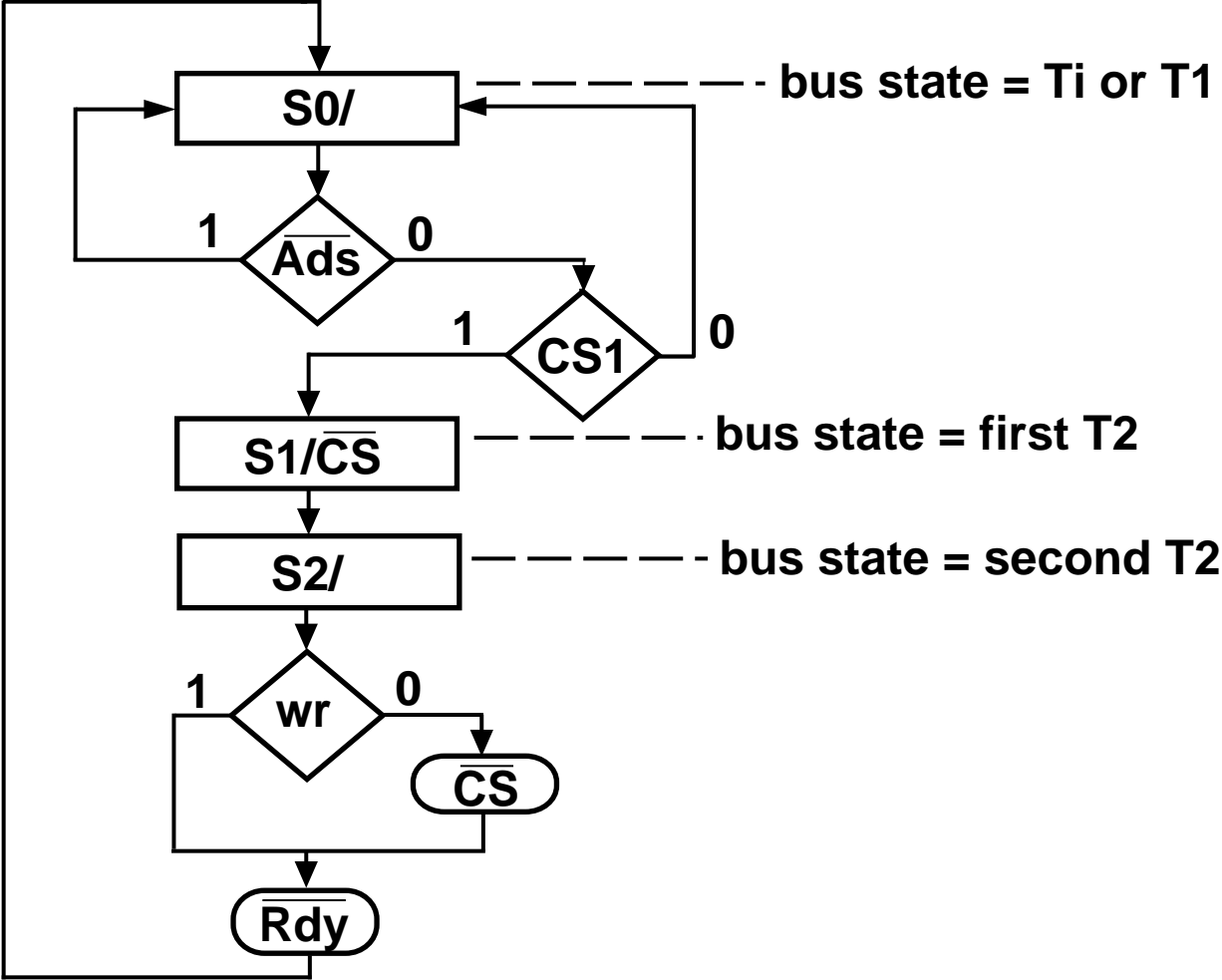



## Figure 9-27(a) VHDL Code for Memory Controller

-- Memory Controller for fast CMOS SRAM w/ one wait state

**entity** memory\_control **is**

**port**(        clk, w\_rb, ads\_b, cs1: **in** bit;

        rdy\_b, we\_b, cs\_b: **out** bit := '1');

**end** memory\_control;

**architecture** behave1 **of** memory\_control **is**

**constant** delay: time := 5 ns;

**signal** state, nextstate: integer **range** 0 **to** 2;

**signal** new\_we\_b, new\_cs\_b, new\_rdy\_b: bit := '1';

## Figure 9-27(b) VHDL Code for Memory Controller

```
begin
  process(state,ads_b,w_rb,cs1)
  begin
    new_cs_b <= '1'; new_rdy_b <= '1'; new_we_b <= '1';
    case state is
      when 0 =>   if ads_b = '0' and cs1 = '1' then nextstate <= 1;
                  else nextstate <= 0;
                  end if;
      when 1 => new_cs_b <= '0'; nextstate <= 2;
      when 2 =>   if w_rb = '1' then new_cs_b <= '1';
                  else new_cs_b <= '0';
                  end if;
      new_rdy_b <= '0'; nextstate <= 0;
    end case;
  end process;

  process(clk)
  begin
    if clk = '1' then state <= nextstate; end if;
  end process;

  we_b <= not w_rb after delay;
  cs_b <= new_cs_b after delay;
  rdy_b <= new_rdy_b after delay;
end behave1;
```

## Figure 9-28(a) VHDL Code for 486 Bus System Test Module

-- Tester for Bus model

**library** BITLIB;

**use** BITLIB.bit\_pack.all;

**use** std.textio.all;

**entity** tester **is**

**port** ( address, w\_data: **out** bit\_vector(31 **downto** 0);

        r\_data: **in** bit\_vector(31 **downto** 0);

        clk, wr, br: **out** bit;

        std, done: **in** bit := '0');

**end** tester;

**architecture** test1 **of** tester **is**

**constant** half\_period: time := 10 ns;

-- 20 ns clock period

**signal** testclk: bit := '1';

**begin**

    testclk <= **not** testclk **after** half\_period;

    clk <= testclk **after** 1 ns;

-- Delay bus clock

    read\_test\_file: **process**(testclk)

**file** test\_file: text **open** read\_mode **is** "test2.dat";

**variable** buff: line;

**variable** dataint, addrint: integer;

**variable** new\_wr, new\_br: bit;

## Figure 9-28(b) VHDL Code for 486 Bus System Test Module

```
begin
  if testclk = '1' and done = '1' then
    if std = '1' then
      assert dataint = vec2int(r_data)
      report "Read data doesn't match data file!"
      severity error;
    end if;
    if not endfile(test_file) then
      readline(test_file, buff);
      read(buff, new_br);
      read(buff, new_wr);
      read(buff, addrint);
      read(buff, dataint);
      br <= new_br;
      wr <= new_wr;
      address <= int2vec(addrint,32);
      if new_wr = '1' and new_br = '1' then
        w_data <= int2vec(dataint,32);
      else w_data <= (others => '0');
      end if;
    end if;
  end if;
end process read_test_file;
end test1;
```

## Figure 9-29(a) VHDL Code for Complete 486 Bus System with Static RAM

```
library IEEE;
use IEEE.std_logic_1164.all;
entity i486_bus_sys is
end i486_bus_sys;

architecture bus_sys_bhv of i486_bus_sys is
--*****
--
--                COMPONENTS
--*****
component i486_bus
    port (    --external interface
        abus: out bit_vector(31 downto 0); dbus: inout std_logic_vector(31 downto 0);
        w_rb, ads_b: out bit; rdy_b, clk: in bit;
        --internal interface
        address, w_data: in bit_vector(31 downto 0);
        r_data: out bit_vector(31 downto 0); wr, br: in bit; std, done:out bit);
end component;
component static_RAM
    generic (constant tAA,tACS,tCLZ,tCHZ,tOH,tWC,tAW,tWP,tWHZ,tDW,tDH,tOW: time);
    port (    CS_b, WE_b, OE_b: in bit;
        Address: in bit_vector(7 downto 0); Data: inout std_logic_vector(7 downto 0));
end component;
component memory_control
    port(    clk, w_rb, ads_b, cs1: in bit;
        rdy_b, we_b, cs_b: out bit);
end component;
```

## Figure 9-29(b) VHDL Code for Complete 486 Bus System with Static RAM

**component** tester

```
    port (    address, w_data: out bit_vector(31 downto 0);
           r_data: in bit_vector(31 downto 0);
           clk, wr, br: out bit;
           std, done: in bit);
```

**end component;**

```
--                                SIGNALS
--*****
    constant decode_delay: time := 5 ns;
    constant addr_decode: bit_vector(31 downto 8) := (others => '0');
    signal cs1: bit;
    -- signals between tester and bus interface unit
    signal address, w_data, r_data: bit_vector(31 downto 0);
    signal clk, wr, br, std, done: bit;
    -- external 486 bus signals
    signal w_rb, ads_b, rdy_b: bit;
    signal abus: bit_vector(31 downto 0);
    signal dbus: std_logic_vector(31 downto 0);
    -- signals to RAM
    signal cs_b, we_b: bit;
--*****
```

## Figure 9-29(c) VHDL Code for Complete 486 Bus System with Static RAM

**begin**

```
bus1: i486_bus port map (abus, dbus, w_rb, ads_b, rdy_b, clk, address,
                        w_data, r_data, wr, br, std, done);
control1: memory_control port map (clk, w_rb, ads_b, cs1, rdy_b, we_b, cs_b);
RAM32: for i in 3 downto 0 generate
    ram: static_RAM
        generic map(25 ns,25 ns,3 ns,3 ns,3 ns,25 ns,
                    15 ns,15 ns,10 ns,12 ns,0 ns,0 ns)
        port map(cs_b, we_b, '0', abus(7 downto 0), dbus(8*i+7 downto 8*i));
    end generate RAM32;
test: tester port map(address, w_data, r_data, clk, wr, br, std, done);
--*****
-- Address decoder signal sent to memory controller
cs1 <= '1' after decode_delay when (abus(31 downto 8) = addr_decode)
    else '0' after decode_delay;
--*****
end bus_sys_bhv
```

**Table 9-3 Test Data for 486 Bus System**

<i>br</i>	<i>wr</i>	<i>addr</i>	Data	Bus action
0	1	7	23	Idle
1	1	139	4863	Write
1	1	255	19283	Write
1	0	139	4863	Read
1	0	255	19283	Read
0	0	59	743	Idle
1	0	139	4863	Read
1	1	139	895	Write
1	0	139	895	Read
1	1	2483	0	Bus hang



# Figure 9-30. Test results for 486 bus system

